

ECG-Amplifier

MB Jass 2009
Daniel Paulus / Thomas Meier

Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT


Operation amplifier (op-amp)

Properties

- DC-coupled
- High gain electronic voltage amplifier
- Inverting / non-inverting input and single output
- Output of the op-amp is usually controlled by negative feedback
- Differential amplifier (just the difference between V_+ and V_- is amplified)

Circuit diagram symbol

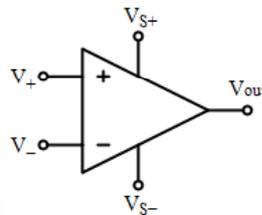- V_+ : non-inverting input
- V_- : inverting input
- V_{out} : output
- V_{S+} : positive power supply
- V_{S-} : negative power supply




Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Ideal op-amp

Properties for an ideal op-amp

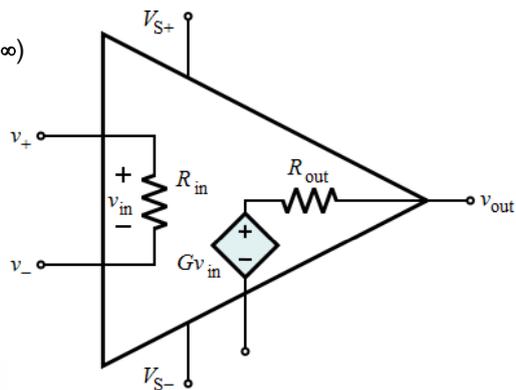- Zero output impedance ($R_{out} = 0$)
- Infinite open-loop gain
- Infinite input impedance ($R_{in} = \infty$)
- Zero offset voltage
- Zero noise




Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Common mode gain

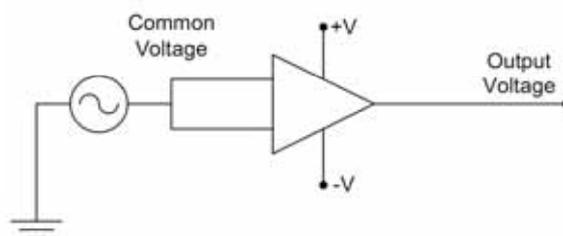- Ideal op-amps amplify only the voltage difference in its inputs
- Real op-amps amplify also voltage that is common to both inputs (common mode gain)
- Minimizing this common mode gain (i.e. maximizing the common mode rejection ratio, 'CMRR') is important for most applications




Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Non-inverting Amplifier

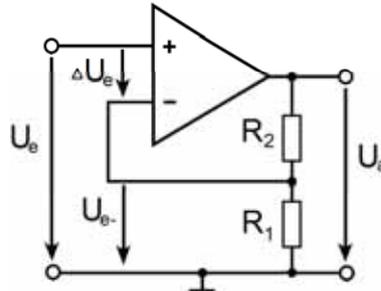- Very high input impedance
- Small output impedance
- Gain: $U_a = (1 + \frac{R_2}{R_1})U_e$
- Amplifies U_e regarding to the ground and not the difference between two different voltages



Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Instrumentation amplifier

- Type of differential amplifier (usually 3 op-amps)
- Input buffers
- Output controlled by negative feedback

Characteristics

- Very low DC offset
- Low drift
- Low signal noise
- Very high open-loop gain
- Very high common-mode rejection ratio
- Very high input impedance

Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Description of the INA 118

INA118:

- Low power, general purpose instrumentation amplifier offering excellent accuracy
- 3 op-amps (small size)
- Current-feedback input provides high gain even at high frequencies



Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

INA118

Electrical Features

- Low offset voltage (50 μV)
- Low temperature drift (0.5 $\mu\text{V}/\text{K}$)
- High common-mode-rejection (110dB) at high gain
- Low quiescent current (350 μA at $\pm 1.35\text{V}$ supply)


- Single external resistor sets any gain from 1 to 10,000
- Internal input protection can withstand up to $\pm 40\text{V}$ without damage

Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Instrumentation amplifier INA118

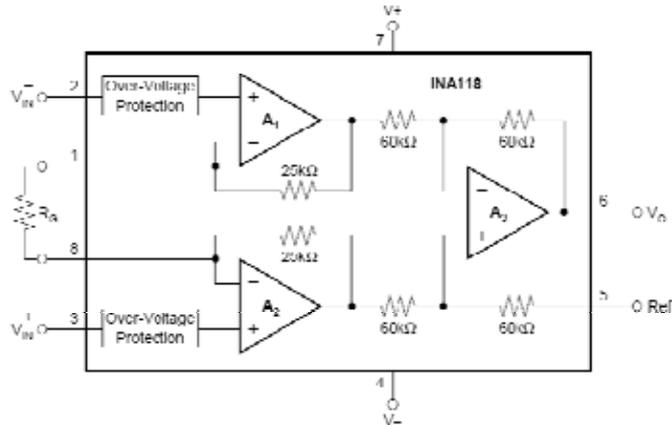- Circuit of the Instrumentation amplifier used in our ECG-circuit




- Gain: $G = 1 + \frac{50k\Omega}{R_G}$

Max Schaldach -
Stiftungsprofessor


Biomedizinische
Technik MSBT

Performance curves (INA118)

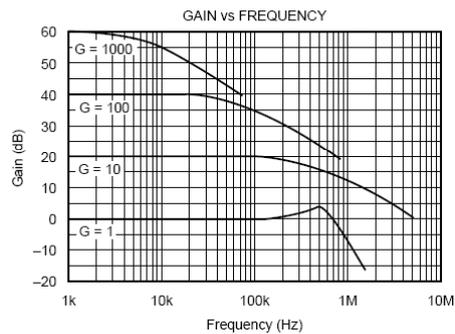Gain of the amplifier plotted
against the frequency



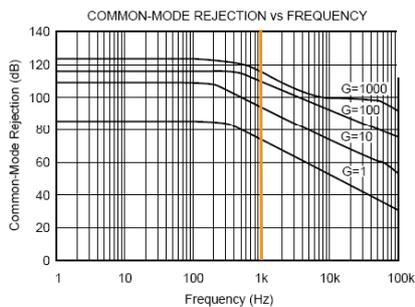Common-mode rejection as a
function of the frequency



Max Schaldach -
Stiftungsprofessor


Biomedizinische
Technik MSBT

Electrocardiogram

Properties of the electric signals on the skin:

- AC signal with bandwidth of 0.05 to 100 Hz, sometimes up to 1 kHz
- About 1 mV peak-to-peak amplitude
- External noise at higher frequencies
- 50/60 Hz interference
- Common-mode voltages (common to all electrodes)

Circuit schematic of an ECG

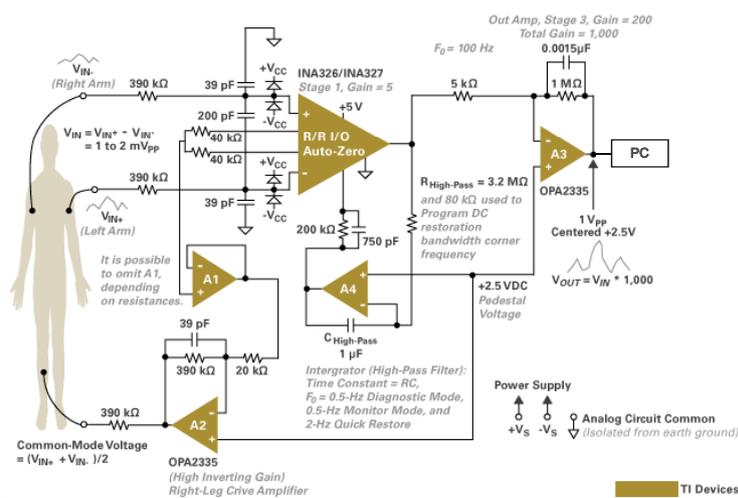

ECG

The common-mode voltage is comprised of two parts:

- 1) 50- or 60-Hz interferences
- 2) DC electrode offset potential

Other noise or higher frequencies within the biophysical bandwidth come from:

- Movement artifacts that change the skin-electrode interface
- Muscle contraction or electromyographic spikes
- Respiration
- Electromagnetic interferences
- Noise from other electronic devices that couple into the input

ECG


- Some noise can be cancelled with a high-input-impedance instrumentation amplifier (INA)
 - removes the AC line noise common to both inputs
 - amplifies the remaining unequal signals present on the inputs



**Let's detect an ECG with our
construction**

Filter

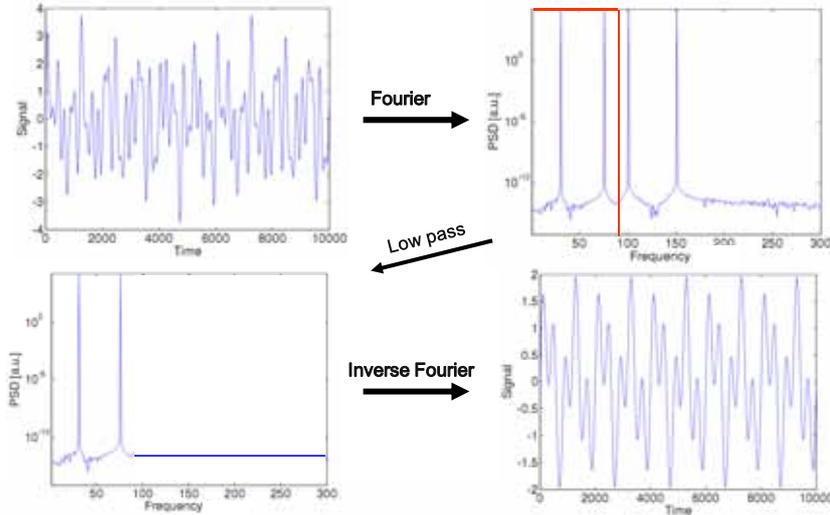
Device for manipulating the frequency content of a given signal



Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Passive analog filter: RC network


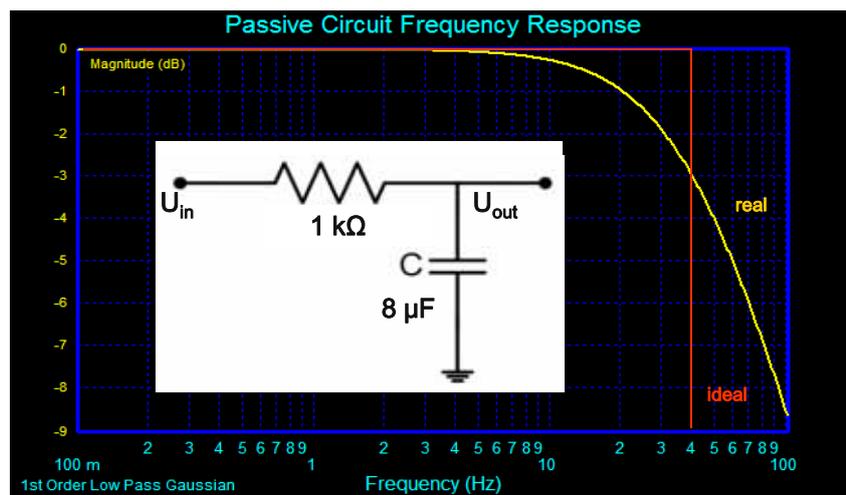


$$\text{Impedance of capacitor: } Z = 1/(\omega C) \rightarrow f_{co} = (RC)^{-1}$$

Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Active analog filter

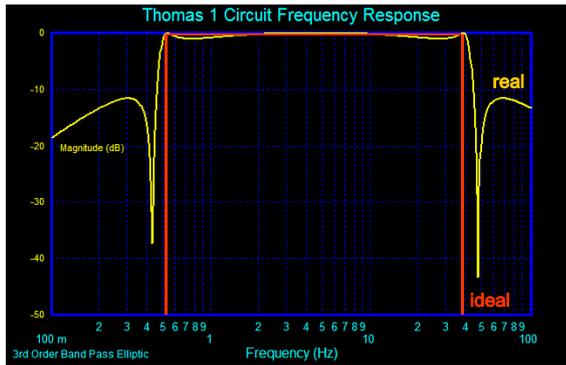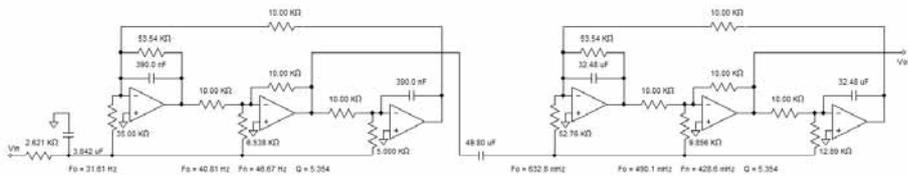


- Complex circuit
- Once it's set up, it's hard to change

Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Fourier Transform

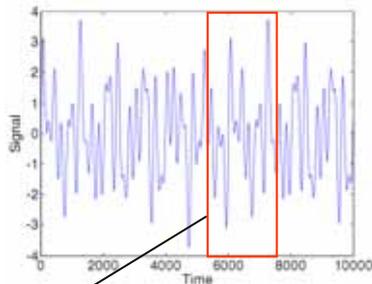- Direct manipulation of frequency content in the frequency domain is suitable for post processing only! (Whole signal has to be stored in memory)
- Possible solution for in-stream processing: windowing



Problems:

- High computational cost
- Frequency spectrum limited by window size

Manipulation in Fourier space

Max Schaldach -
Stiftungsprofessor


Biomedizinische
Technik MSBT

Convolution

Possibility: Operating in time domain

- Bring transfer function to time domain by inverse Fourier Transform (Impulse response)
- Cut function to realise convolution of impulse response & signal as sum
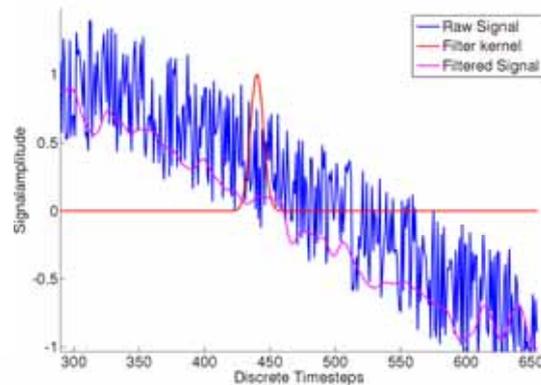
$$Y(t) = \int_{-\infty}^{\infty} T(\tau) \cdot X(t - \tau) d\tau$$




Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Implementation: FIR

- Simple implementation:
convolution implemented as sum
- h is the filter kernel of length q
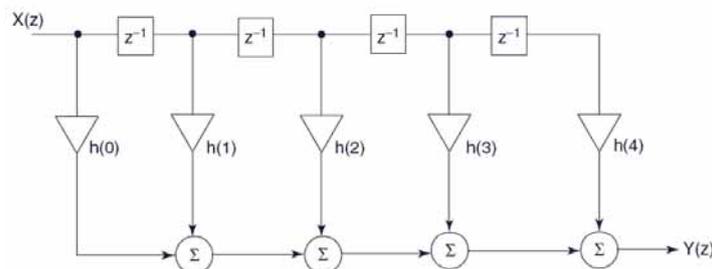
$$Y(z) = \sum_{m=0}^q h(m) \cdot X(z - m)$$



Major drawback:

very long filters necessary to achieve good performance

Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Implementation: IIR


Recursive implementation:

$$Y(z) = \frac{1}{a_0} \left(\sum_{i=0}^p d_i X(z-i) - \sum_{j=0}^q g_j Y(z-j) \right)$$

both input and response are considered

Advantage:

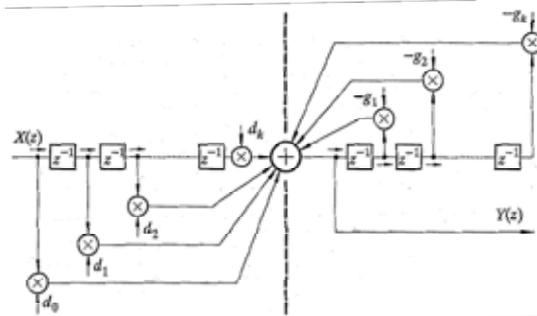
Less coefficients required in comparison to FIR filters to get same performance



Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Digital Filter: Transfer function

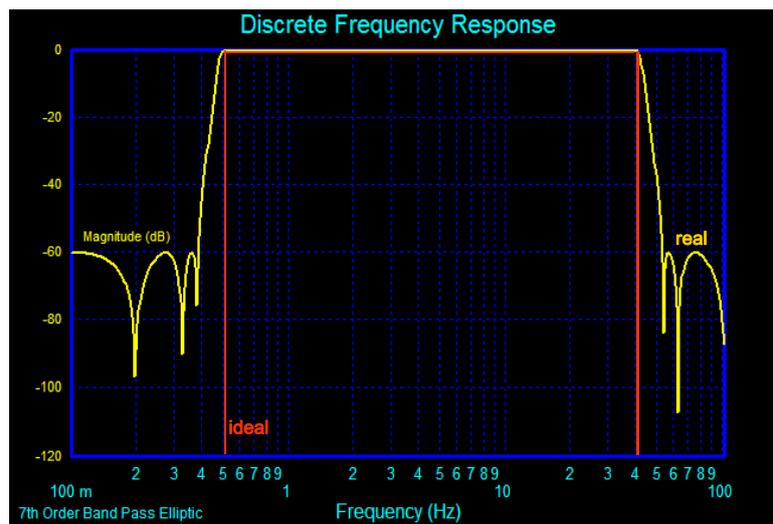

Max Schaldach -
Stiftungsprofessor

Biomedizinische
Technik MSBT

Advantages/Disadvantages

Advantages

- Digital filters can realise frequency responses practically not achievable with analog filters
- No tolerance of circuit components
- No complex circuitry (just a number of coefficients needed)

Disadvantages

- FIR filters need to be large to be effective (many operations)
- IIR filters may be unstable because of feed back loop
- The ADC stage creates deterministic quantisation error which is due to digital storage and computation limitations
- sample rate limitation (analog filters do not have to sample!)
- Filter design is not a simple task