

Extended Applications of Current Source Modeling [1]

Melanie Kimmel
Technische Universität München


[1] Based on “Accurate Timing and Noise Analysis of Combinational and Sequential Logic Cells Using Current Source Modeling” by Shahin Nazarian, Hanif Fatemi and Massoud Pedram

Outline

- Motivation
- Basics
 - MOSFET - Transistor model
 - Capacitive cross-talk noise
- Blade/Razor
- Combinatorial Model
 - Inverter
 - Transmission Gate

- Sequential Model (CMOS Latch)
 - Transparent Mode
 - Opaque Mode
 - Complete Model
- Summary

Motivation

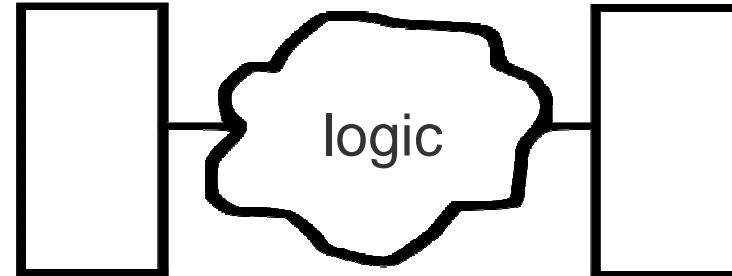


- Feature sizes getting smaller (layout geometries < 65 nm)
 - Increasing packing density and frequency
 - Increasing effect of analog effects
- Need for an accurate model to do timing analysis

→ **Current Source Model** ←


Capacitive Crosstalk Noise

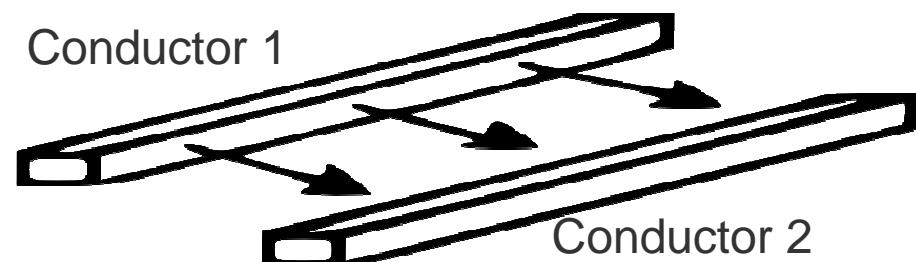- Interconnection of logic cells
- Analog effects are regarded as noise (“capacitive crosstalk noise”)
- Different input voltage waveforms influence the delay of the cells
 - The model has to be able to deal with any noisy input voltage waveform and with any arbitrary load




Transistor Model

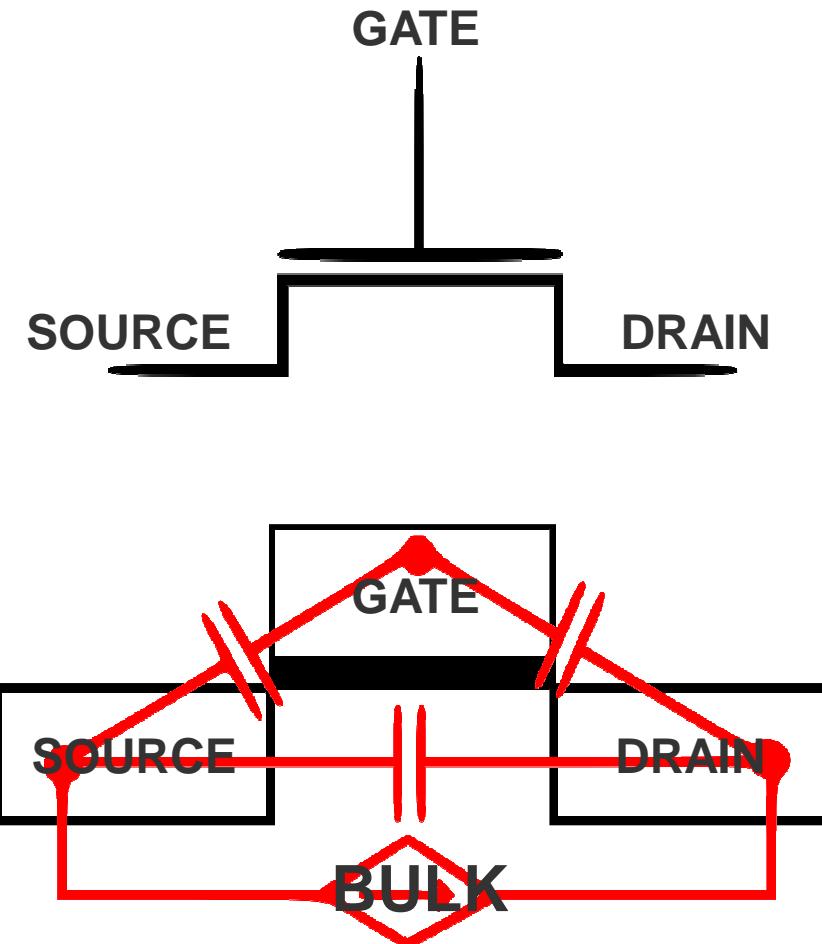- Basis for all Current Source Models
- Used to derive Combinational/Sequential Models
- Interconnection of NMOS/PMOS Transistors and simplification



Blade/Razor [2]

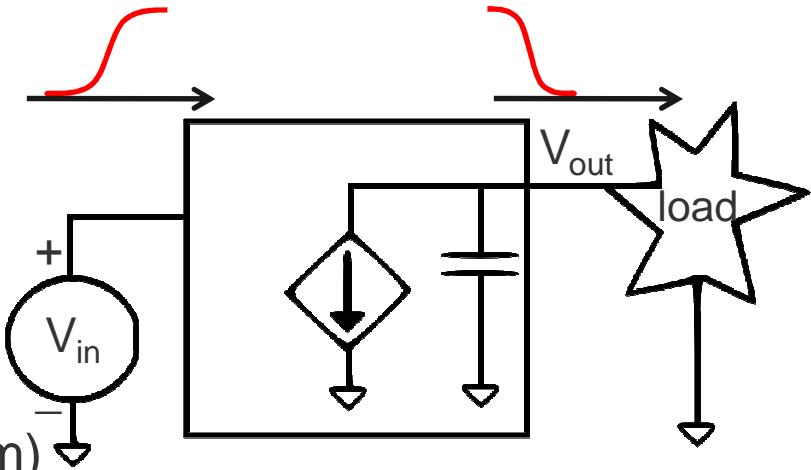- Blade = Current Source Model
- Razor = interconnect model
(algorithm to calculate output waveform)





- First model that can deal with arbitrary Input/Output Voltage and arbitrary loads
- Voltage Controlled Current Source, internal capacitance and input waveform timeshift

[2] As introduced in “Blade and Razor: Cell and Interconnect Delay Analysis Using Current-Based Models” by John Croix and D.F.Wong


Combinatorial Model

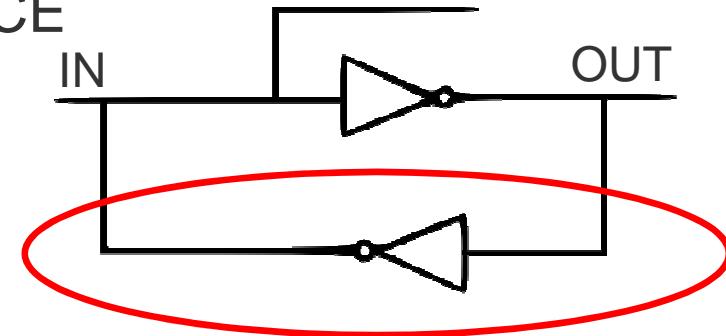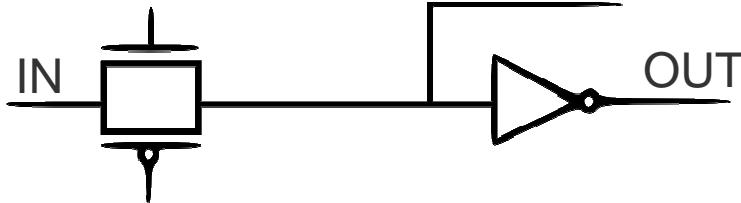- For any CMOS logic cell
- No feedback loops (output only dependent on input)
- Calculate output to an arbitrary input voltage
 - combinatorial
 - sequential
- Result almost as accurate as SPICE



Inverter

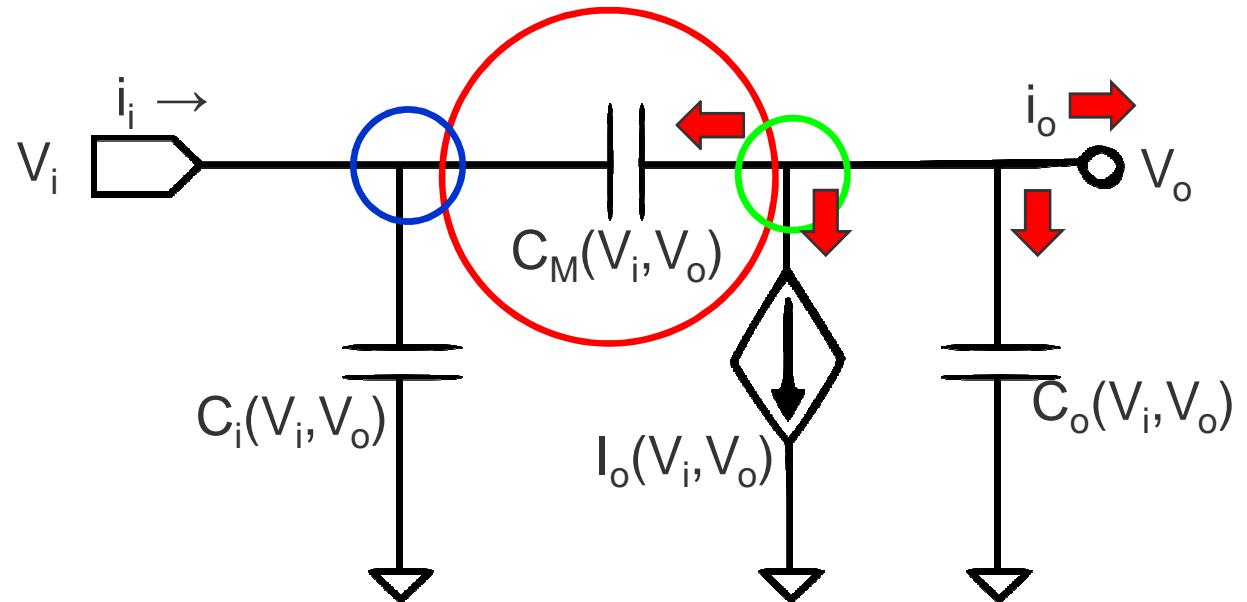Main Difference to existing CSMs:
Capturing parasitic effects between input and output node!



Equations for the current:

$$(I1) \quad i_o + I_o(V_i, V_o) + (C_o(V_i, V_o) + C_M(V_i, V_o)) \frac{dV_o}{dt} - C_M(V_i, V_o) \frac{dV_i}{dt} = 0$$


$$(I2) \quad i_i - (C_i(V_i, V_o) + C_M(V_i, V_o)) \frac{dV_i}{dt} + C_M(V_i, V_o) \frac{dV_o}{dt} = 0$$

Characterization of I_o


- Connect dc-voltage source to V_i and V_o (swept from $-\Delta$ to $V_{DD} + \Delta$)

$$(I1) i_o + I_o(V_i, V_o) + \cancel{\left(C_o(V_i, V_o) + C_M(V_i, V_o) \right)} \frac{dV_o}{dt} - \cancel{C_M(V_i, V_o)} \frac{dV_i}{dt} = 0$$

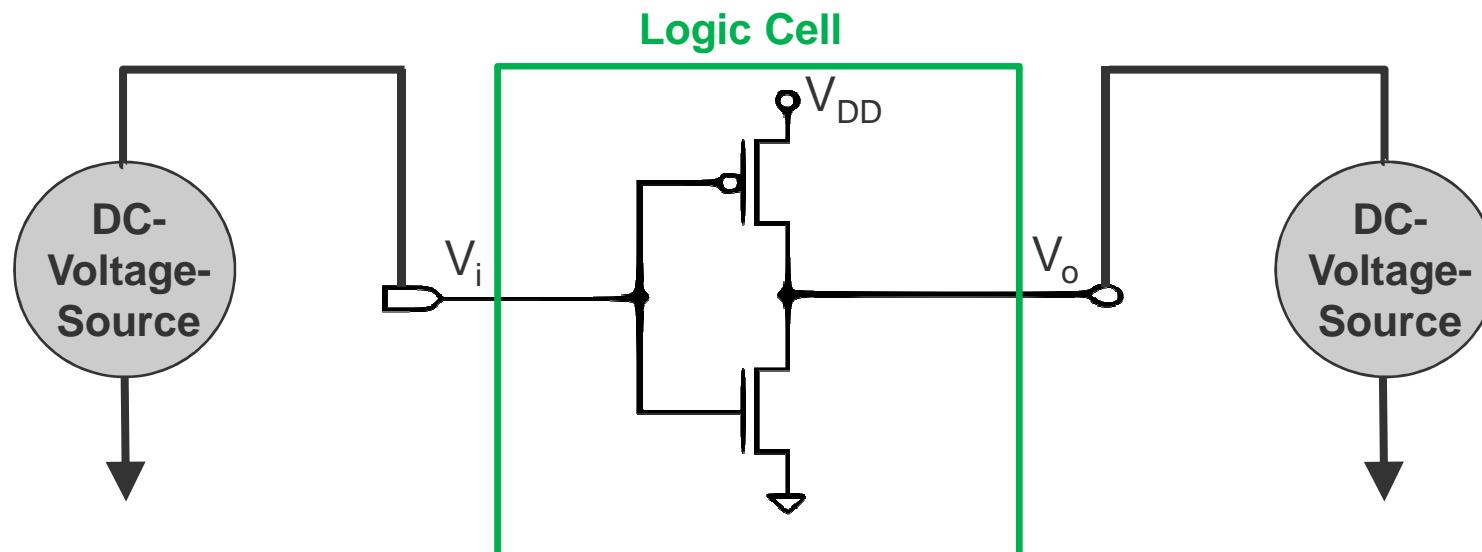- Measure i_o to get value of $I_o(V_i, V_o)$



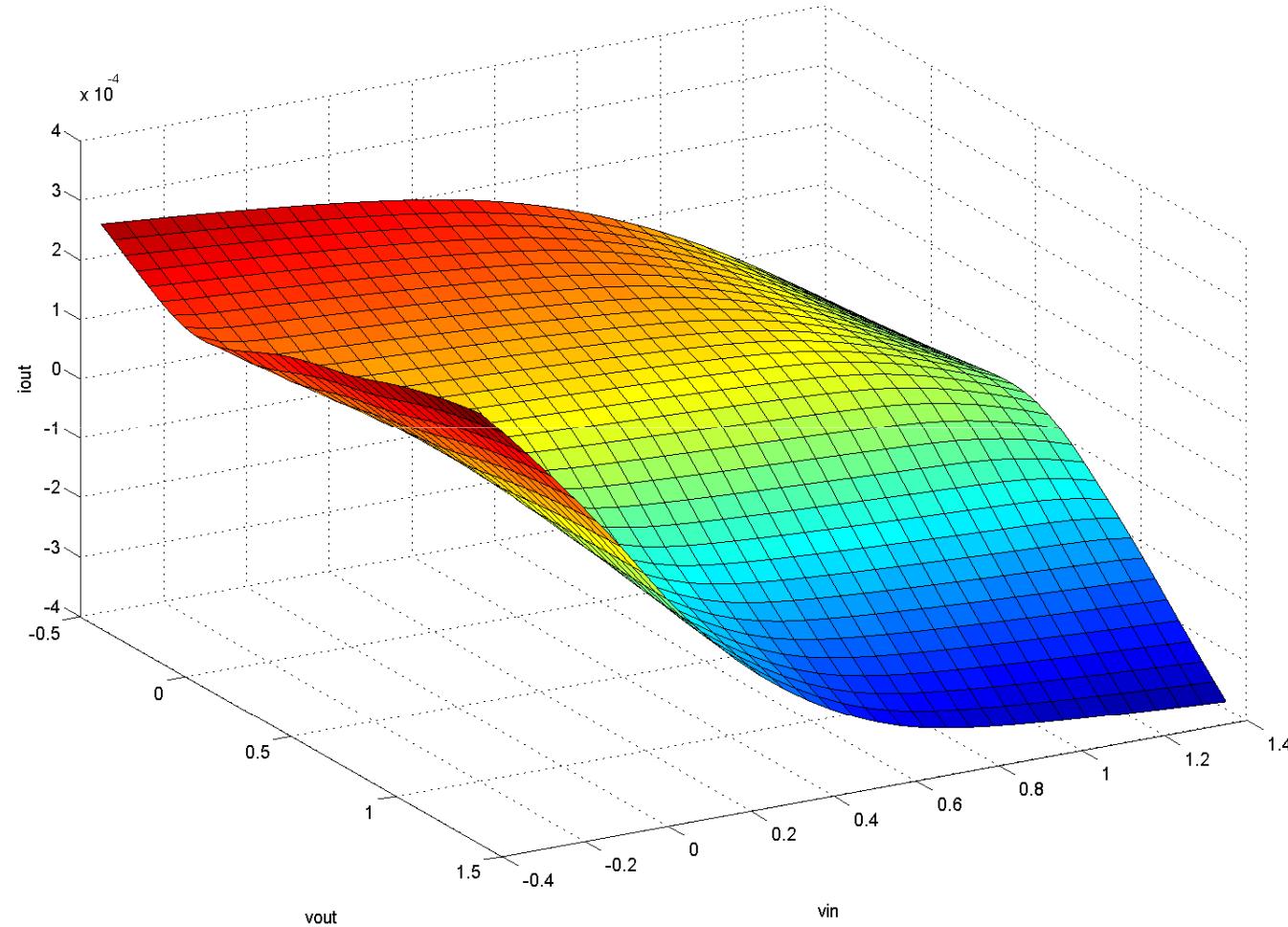Characteristic Values of the Current Source




Characterization of C_M


- Connect dc-voltage source to V_o (swept from $-\Delta$ to $V_{DD}+\Delta$)
- Connect V_i to a saturated ramp

$$(I1) i_o + I_o(V_i, V_o) + \cancel{\left(C_o(V_i, V_o) + C_M(V_i, V_o) \right)} \frac{dV_o}{dt} - C_M(V_i, V_o) \frac{dV_i}{dt} = 0$$

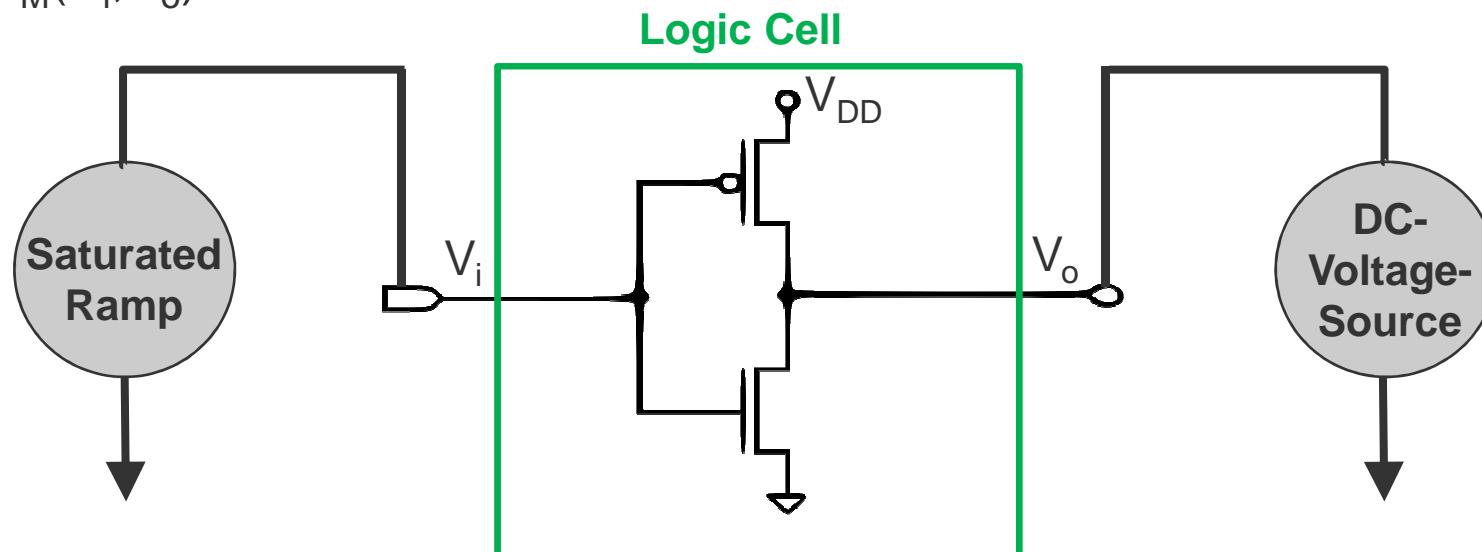- Measure i_o (I_o already characterized) to calculate the value of $C_M(V_i, V_o)$



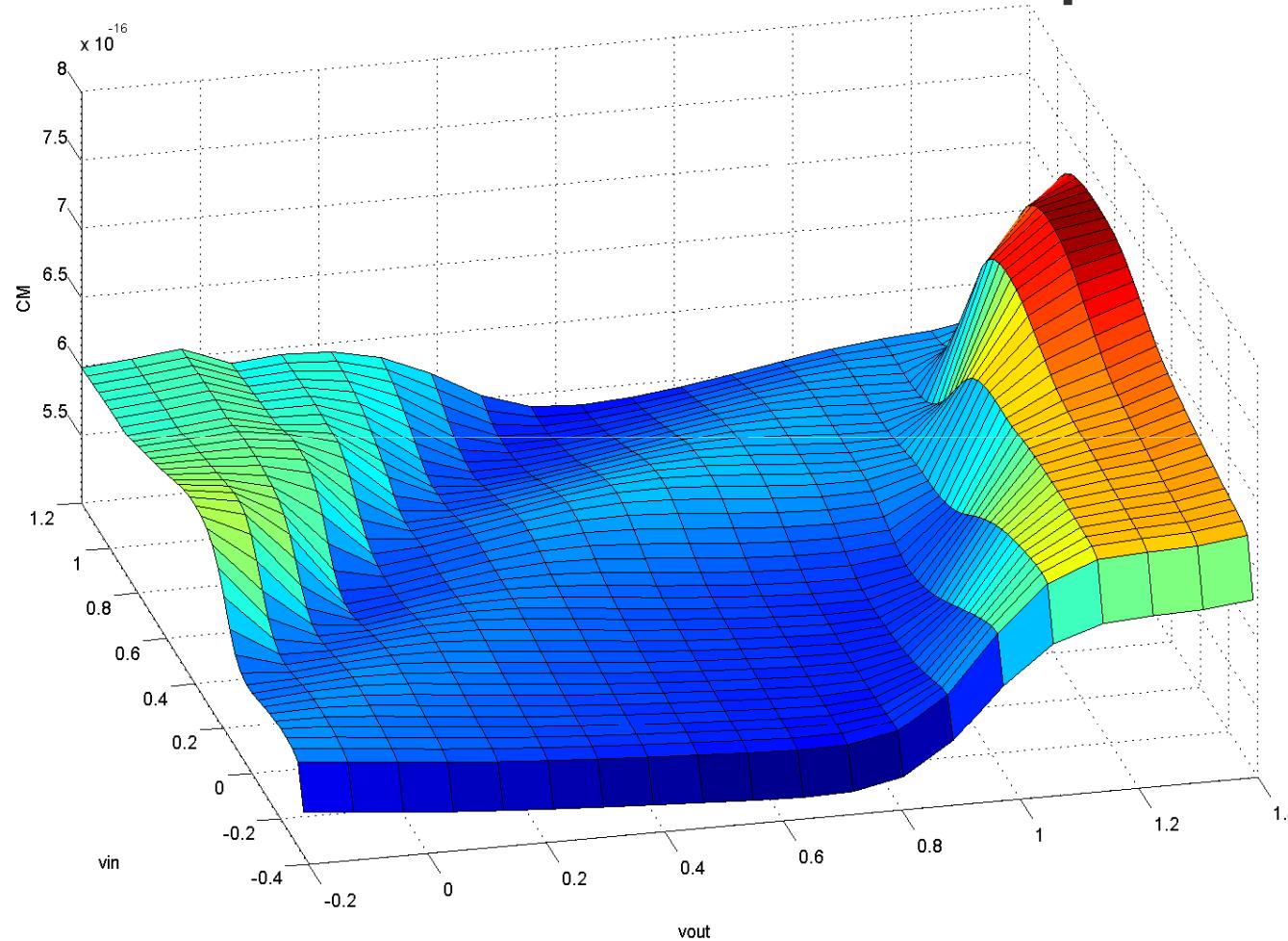Characteristic Values of the Miller Capacitance




Characterization of C_i


- Connect dc-voltage source to V_o (swept from $-\Delta$ to $V_{DD}+\Delta$)
- Connect V_i to a saturated ramp

$$(I2) i_i - (C_i(V_i, V_o) + C_M(V_i, V_o)) \frac{dV_i}{dt} + C_M(V_i, V_o) \cancel{\frac{dV_o}{dt}} = 0$$

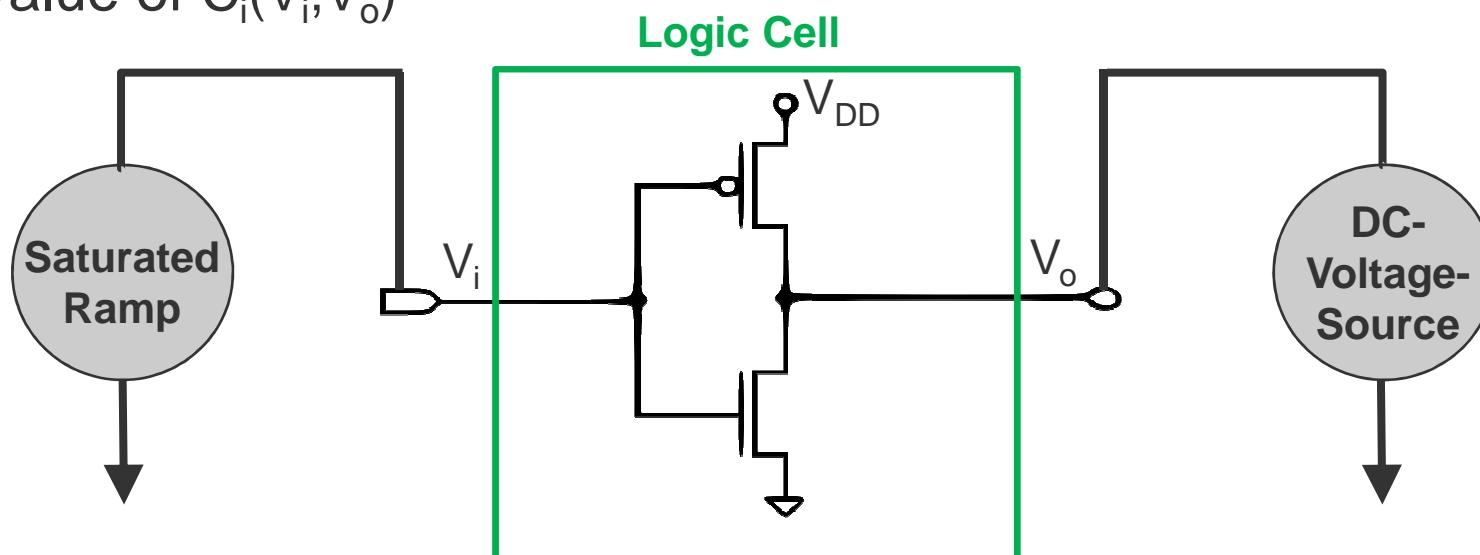- Measure i_i (I_o and C_M already characterized) to calculate the value of $C_i(V_i, V_o)$



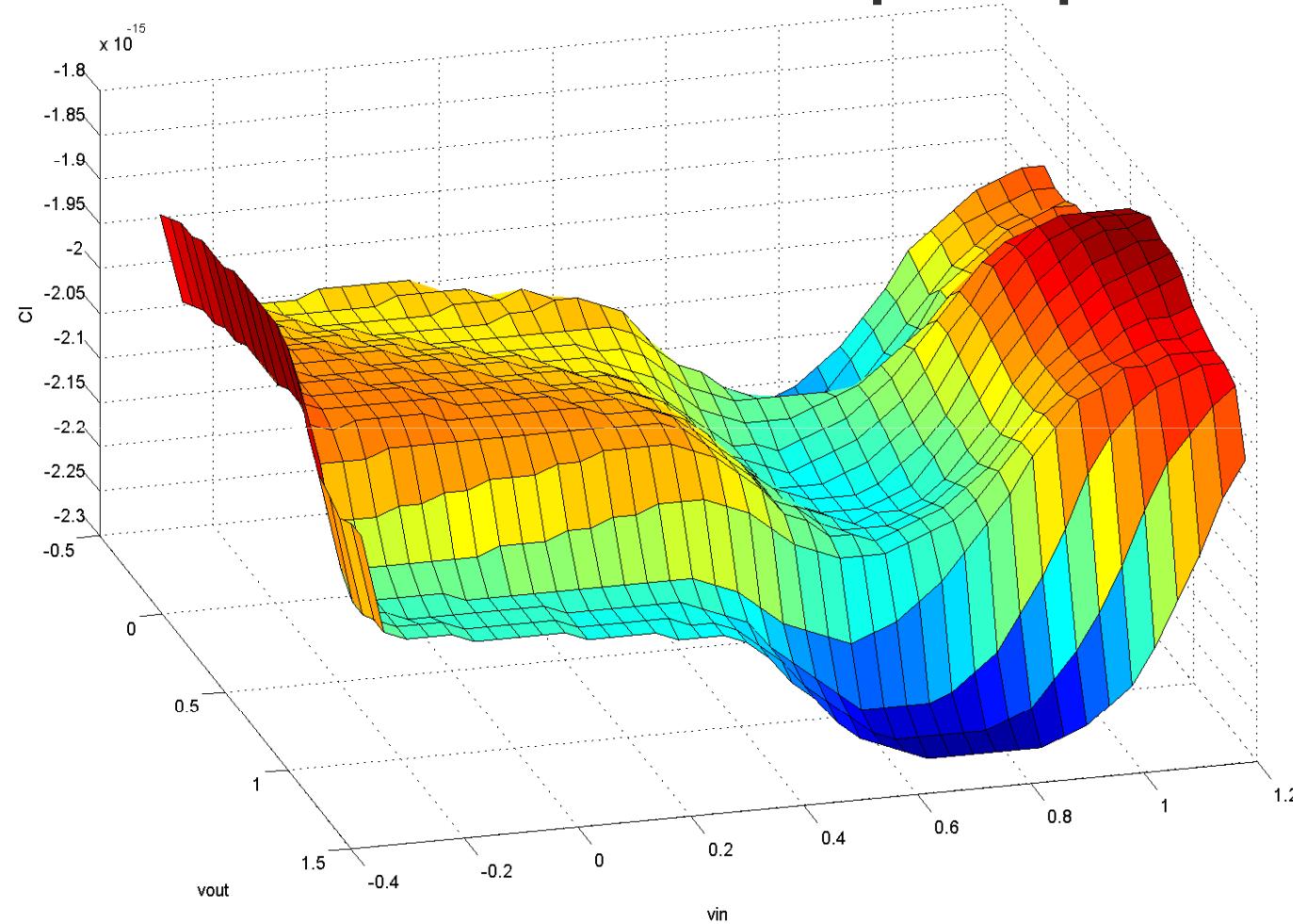Characteristic Values of the Input Capacitance




Characterization of C_o


- V_i connected to dc-voltage, V_o connected to a saturated ramp)

$$(I1) i_o + I_o(V_i, V_o) + (C_o(V_i, V_o) + C_M(V_i, V_o)) \frac{dV_o}{dt} - \cancel{C_M(V_i, V_o)} \frac{dV_i}{dt} = 0$$

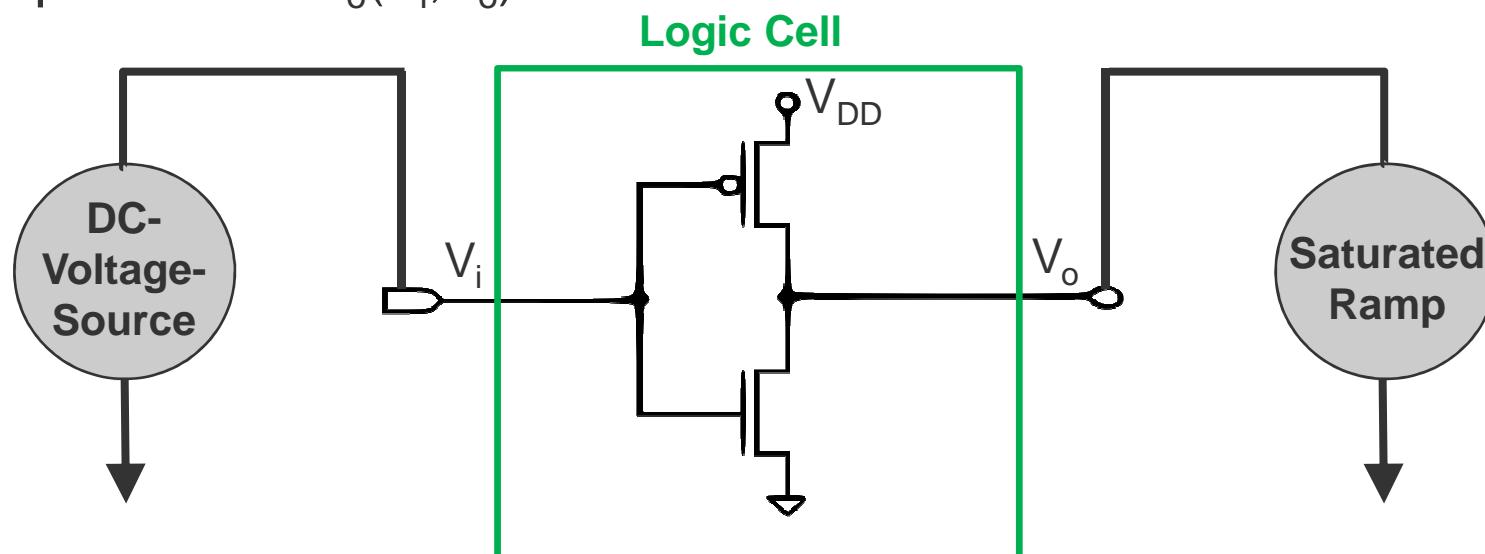- Measure i_o (I_o and C_M already characterized) and solve equation for $C_o(V_i, V_o)$




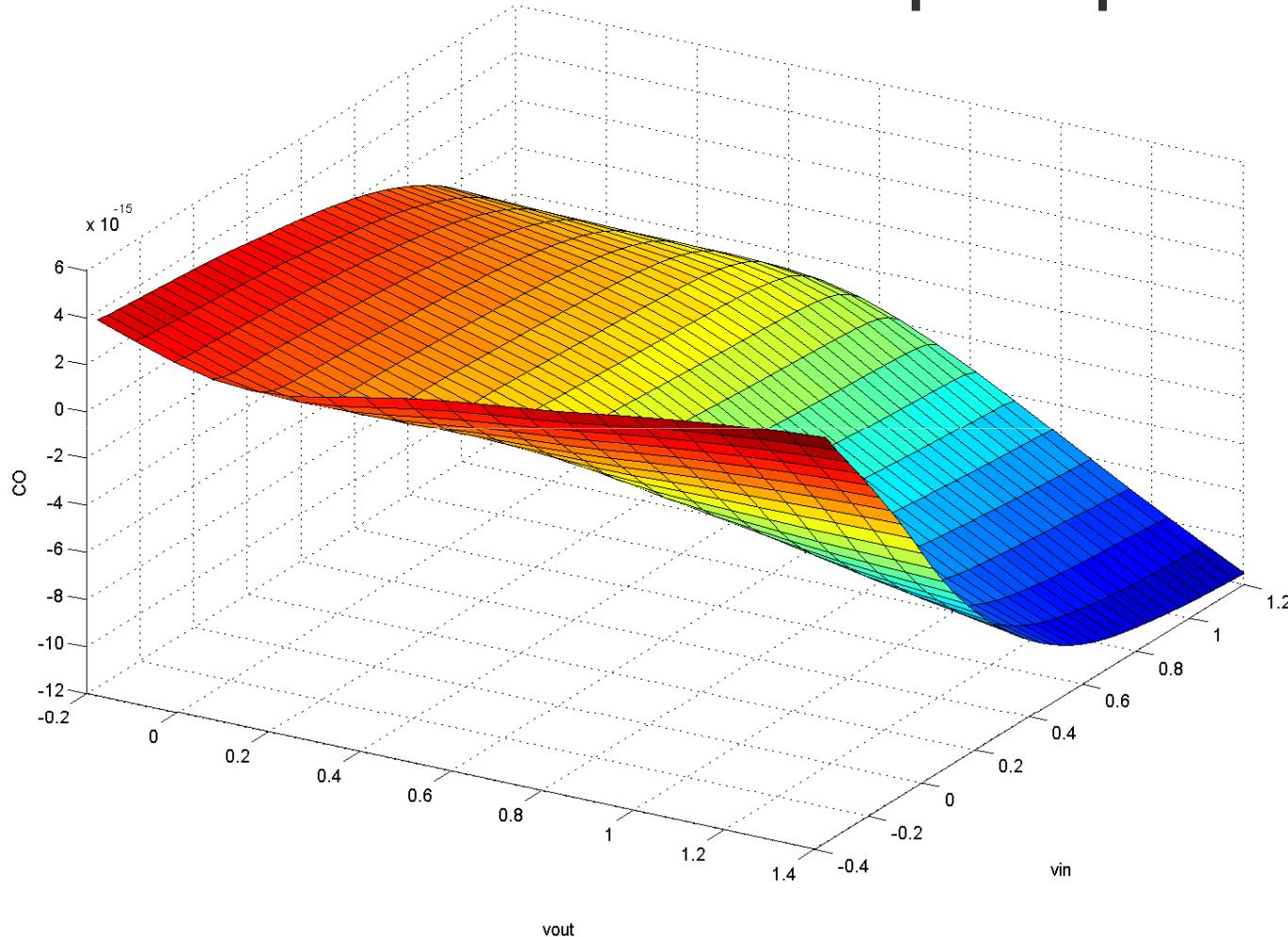
Characteristic Values of the Output Capacitance




Transmission Gate

3 Cases:

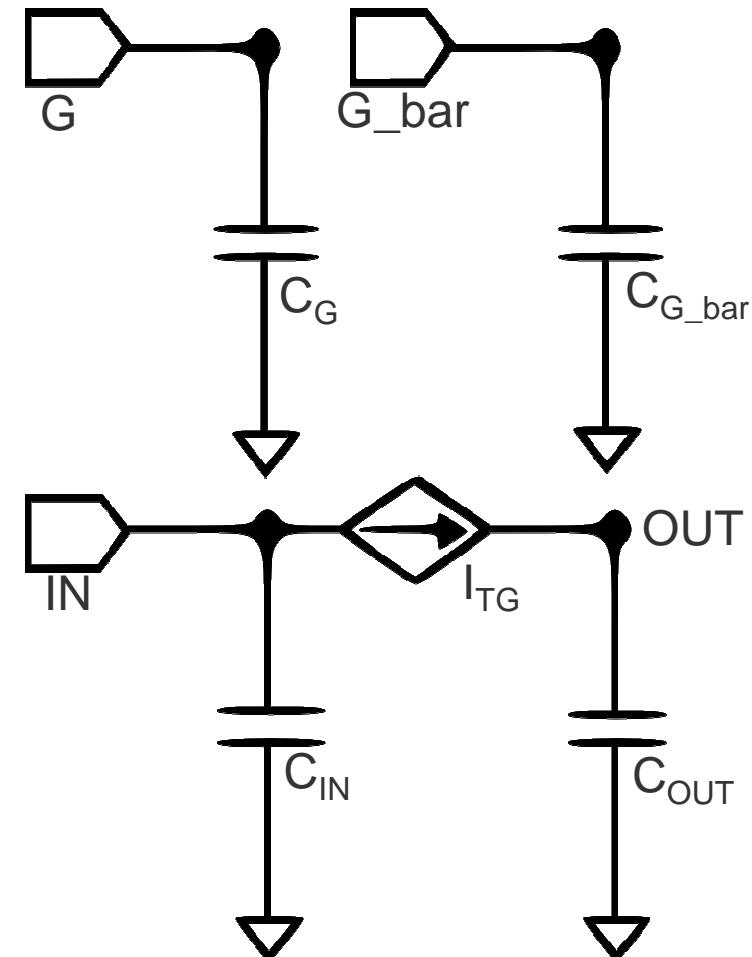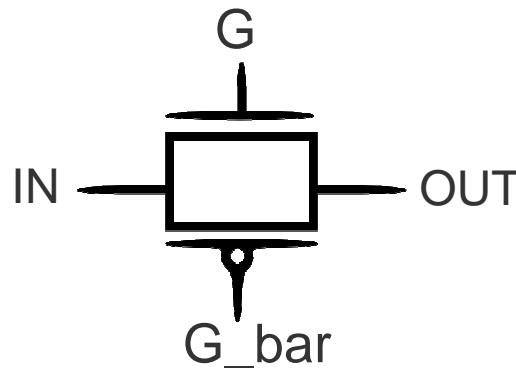- OFF
- Conducting ($OUT = IN$)
- Rising/Falling Transition



CSM for the Transmission Gate

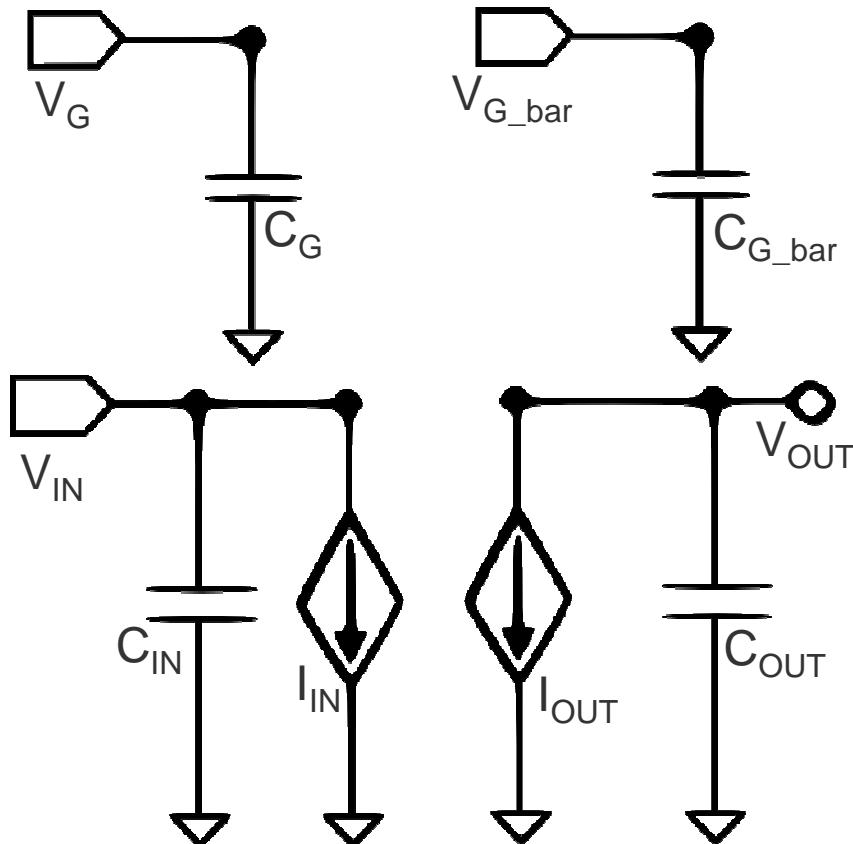

Components:

$$C_G = C_G(V_{IN}, V_{OUT}, V_G)$$

$$C_{G_bar} = C_{G_bar}(V_{IN}, V_{OUT}, V_{G_bar})$$

$$C_{IN} = C_{IN-G}(V_{IN}, V_{OUT}, V_G) + \\ C_{IN-G_bar}(V_{IN}, V_{OUT}, V_{G_bar})$$


$$C_{OUT} = C_{OUT-G}(V_{IN}, V_{OUT}, V_G) + \\ C_{OUT-G_bar}(V_{IN}, V_{OUT}, V_{G_bar})$$

$$I_{IN} = I_{IN-G}(V_{IN}, V_{OUT}, V_G) + \\ I_{IN-G_bar}(V_{IN}, V_{OUT}, V_{G_bar})$$

I_{TG} and I_{OUT} analog


Sequential Model

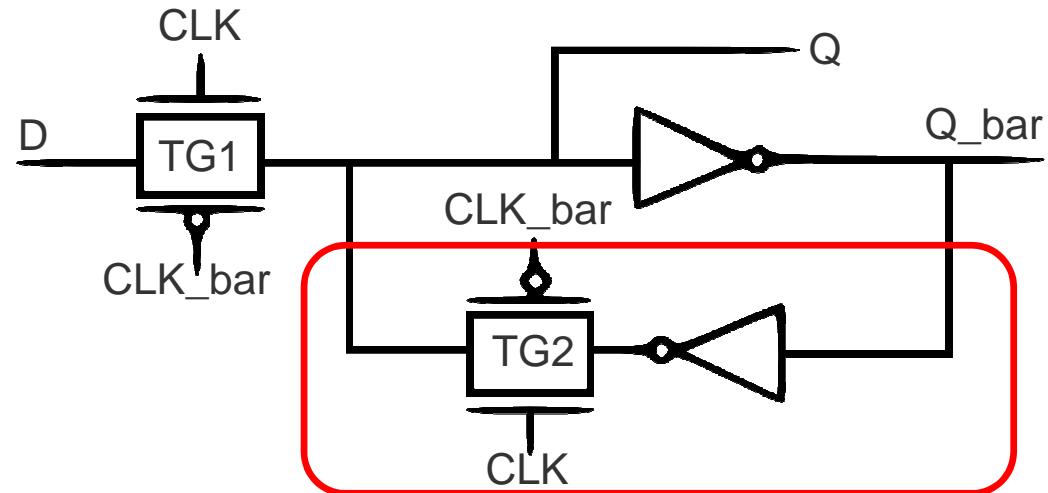- Combination of combinatorial models
- Feedback loops
 - noise can be magnified
- Example: Latch (3 possible modes)
 - Transparent
 - Opaque
 - Transition




Transparent Mode

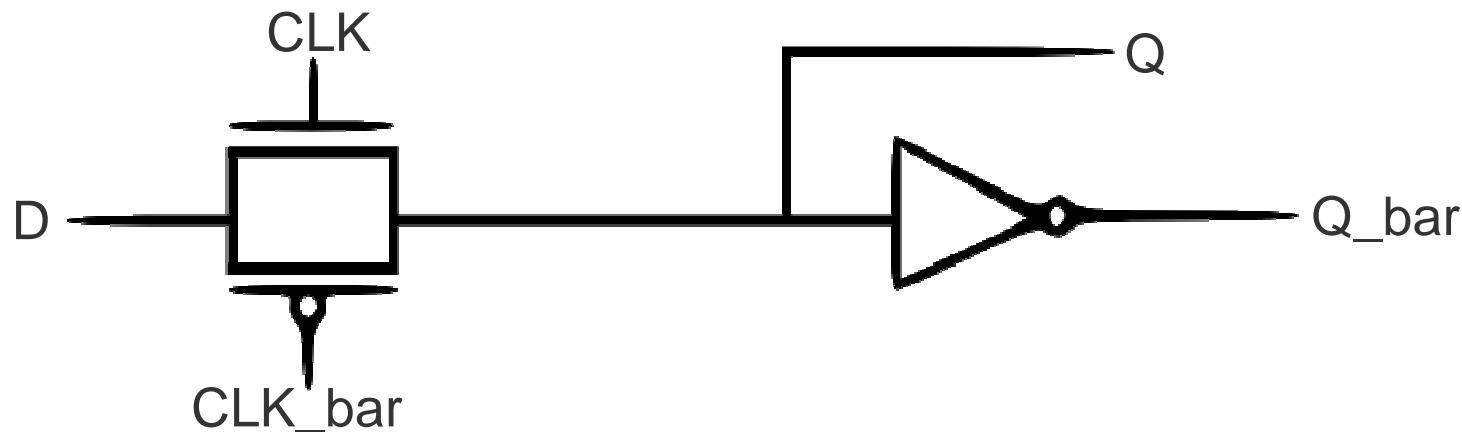- $\text{CLK} = 1$
- TG1 conducts and TG2 is off
- No feedback loop
- $Q = D$




Derivation of the CSM

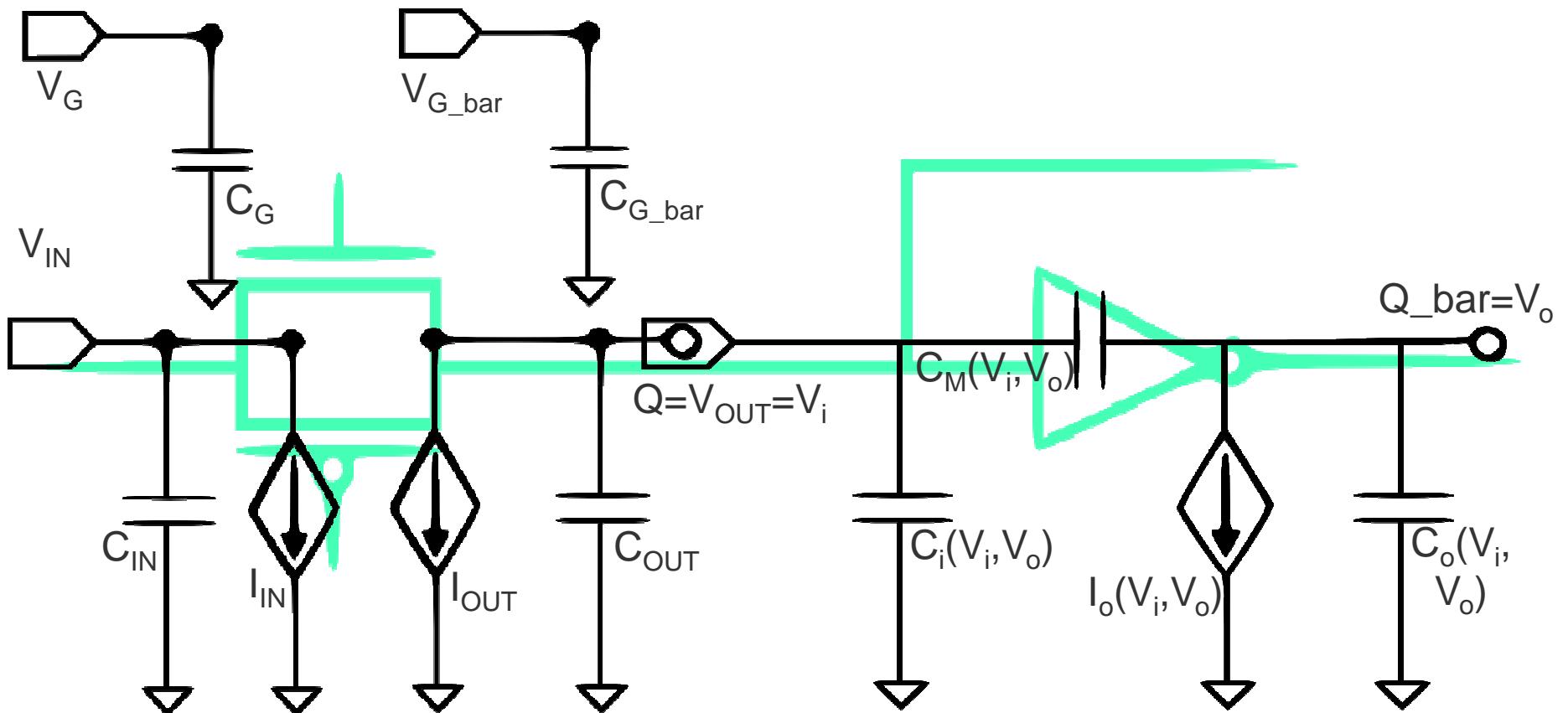

CSM for Latch in Transparent Mode


$$I_{Q-TG1} = I_{Q-CLK_bar}(V_D, V_Q, V_{CLK_bar}) + I_{Q-CLK}(V_D, V_Q, V_{CLK})$$
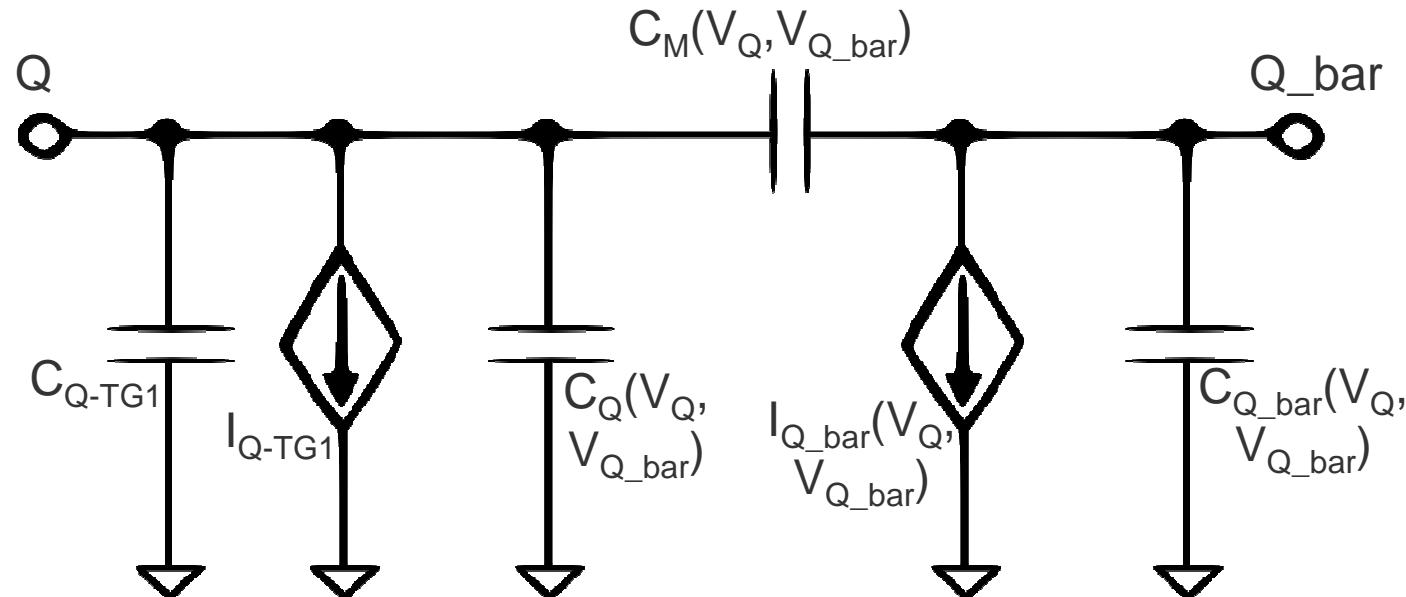
$$C_{Q-TG1} = C_{Q-CLK_bar}(V_D, V_Q, V_{CLK_bar}) + C_{Q-CLK}(V_D, V_Q, V_{CLK})$$




Opaque Mode

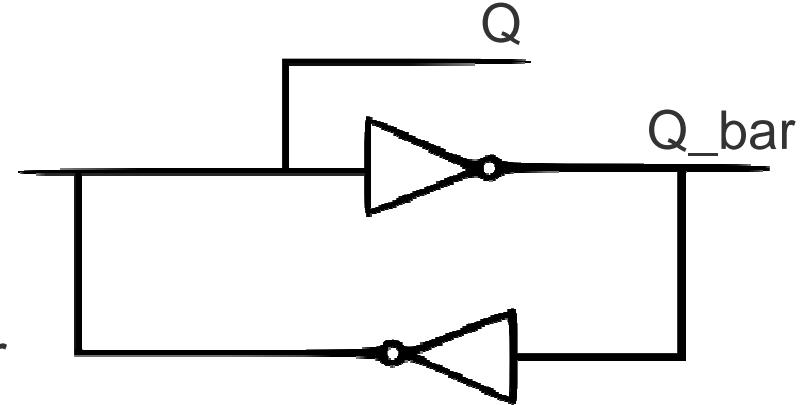- $\text{CLK} = 0$
- TG2 conducts and TG1 is off
- Disconnected input data D
- Q and Q_{bar} stabilize each other




CSM for Latch in Opaque Mode

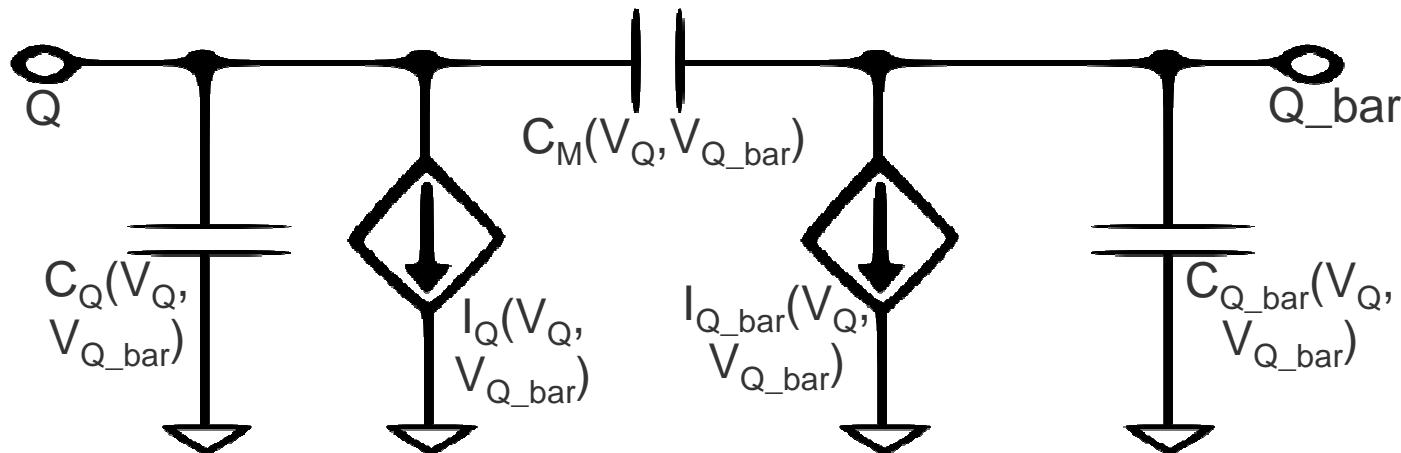


Transition Mode

- CLK in Transition (rising or falling slope)
- Both TGs partially conducting
- All components influence output

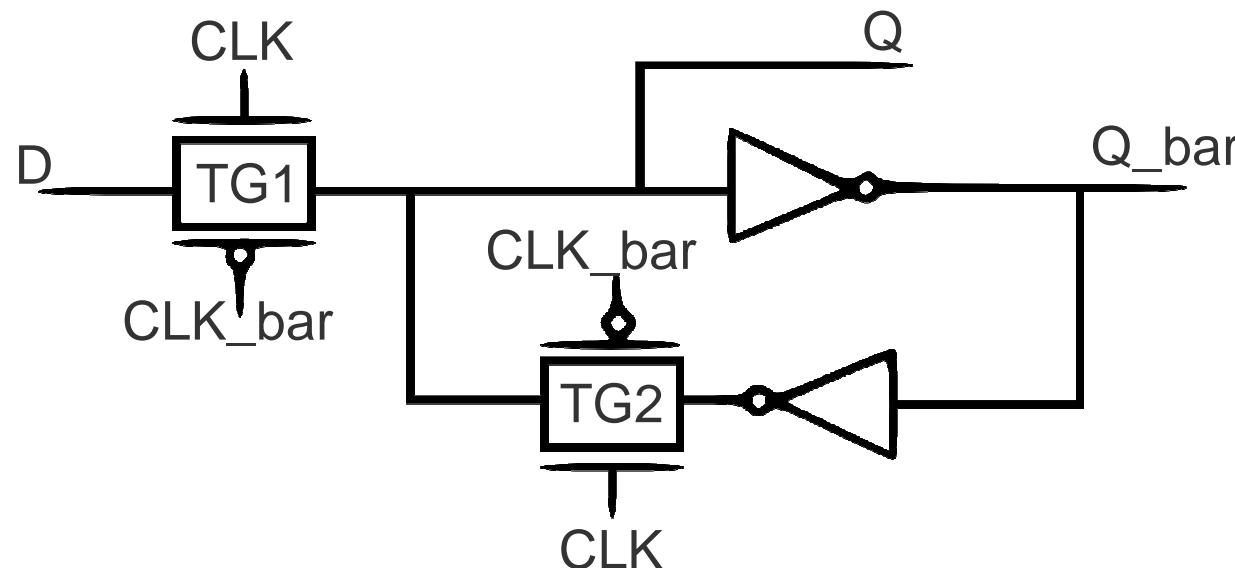→ same CSM as complete model for the latch



Complete Model

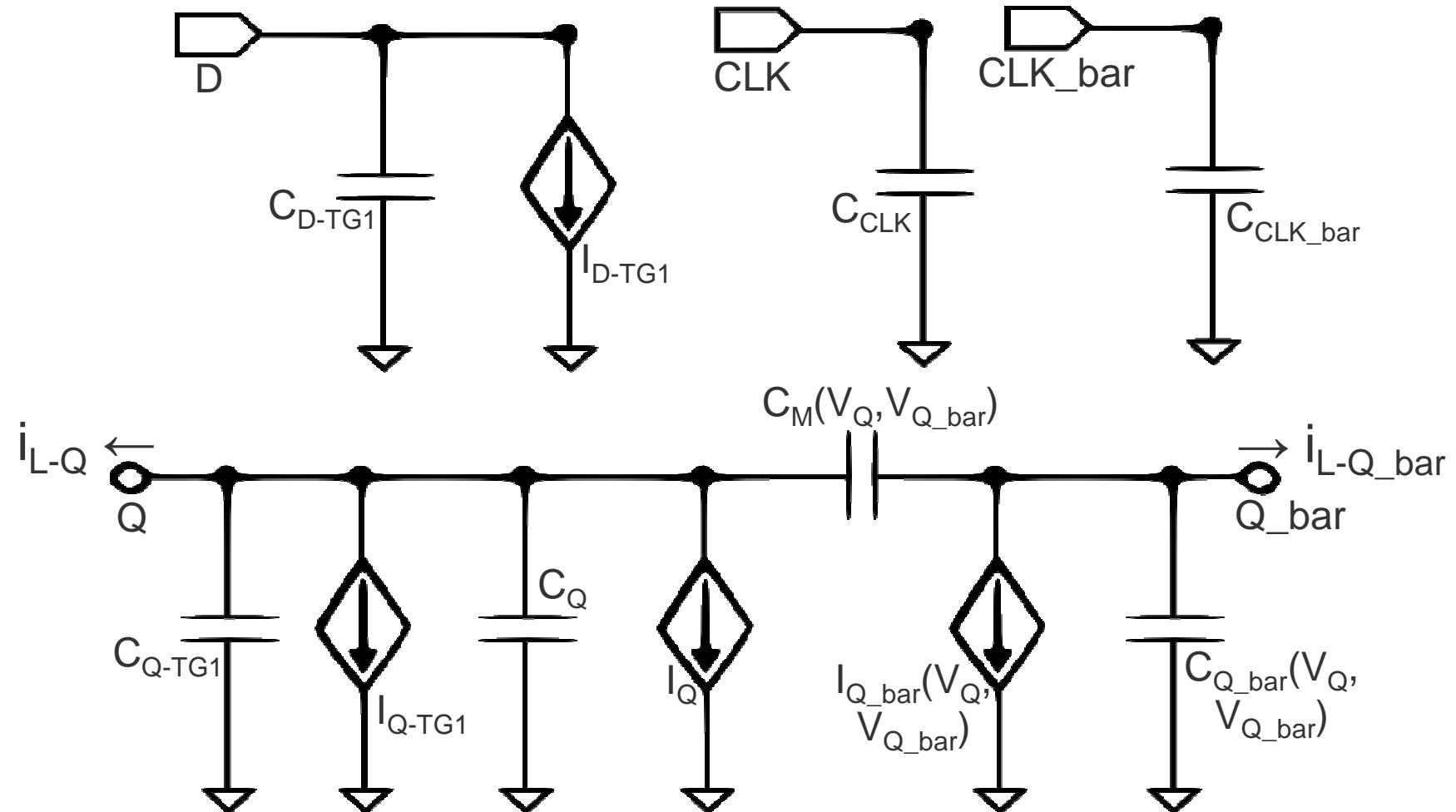

Summary

- New Current Source Model for Combinational Logic Cells
- Derivation of a model for Sequential Logic Cells
- Possibility of modeling noise effects
- Possibility of accurately calculating the output voltage to any arbitrarily shaped input voltage

BACKUP

Output Calculation (Inverter)


$$(I1) i_o + I_o(V_i, V_o) + (C_o(V_i, V_o) + C_M(V_i, V_o)) \frac{dV_o}{dt} - C_M(V_i, V_o) \frac{dV_i}{dt} = 0$$

- All parameters determined as a function of V_o and V_i
- Arbitrary load connected to V_o
- i_o is a function of V_o and the load
- Connect arbitrary input voltage to V_i

→ solve differential equation to determine V_o (Euler)

Characterization of the CSM for the latch

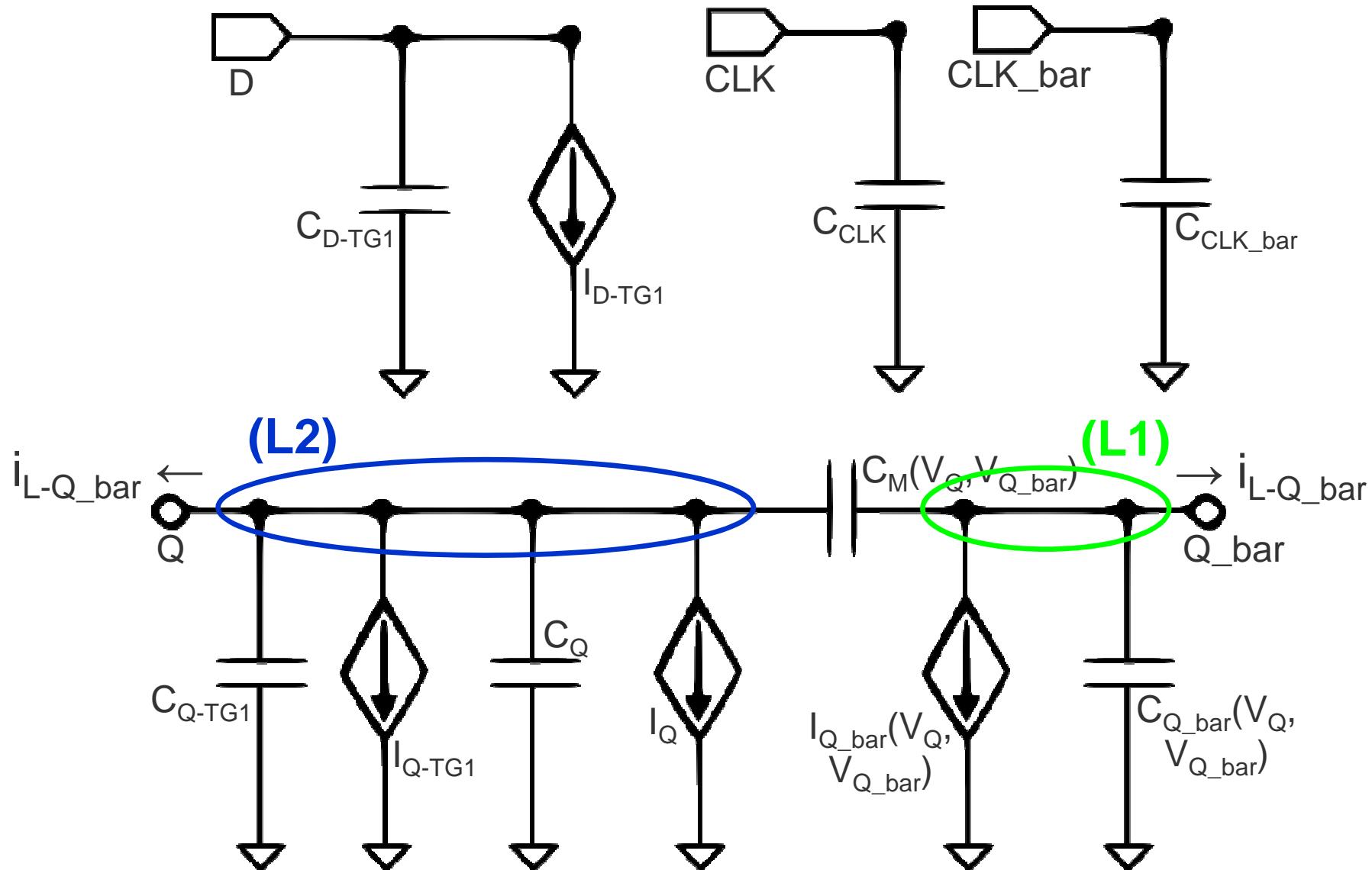- Start by characterizing TG1
- Attach voltage sources to Q, Q_bar, CLK and CLK_bar
- Step by step all capacitances and currents in the 3 modes are characterized



Output Calculation (Complete Latch)

(L1)

$$i_{L-Q_bar} + I_{Q_bar}(V_Q, V_{Q_bar}) - C_M(V_Q, V_{Q_bar}) \frac{dV_Q}{dt} + [C_M(V_Q, V_{Q_bar}) + C_{Q_bar}(V_Q, V_{Q_bar})] \frac{dV_{Q_bar}}{dt} = 0$$

(L2)

$$i_{L-Q} + I_Q + I_{Q-TG1} - C_M(V_Q, V_{Q_bar}) \frac{dV_{Q_bar}}{dt} + [C_M(V_Q, V_{Q_bar}) + C_Q + C_{Q-TG1}] \frac{dV_Q}{dt} = 0$$

- All parameters determined as a function of V_Q and V_{Q_bar}
- Arbitrary load connected to Q and/or Q_bar
- i_{L-Q_bar} / i_{L-Q} is a function of the two voltages and the load
- Connect arbitrary input voltage to D (effects I_{Q-TG1} and C_{Q-TG1})

→ solve differential equation to determine V_Q and V_{Q_bar} (Euler)